

**NEW**  
**3-Tier**  
**2015**  
**ELECTRONICS**  
**(General)**  
**PAPER—III**  
**(PRACTICAL)**

*Full Marks : 100*

*Time : 3 Hours*

*The figures in the margin indicate full Marks.*

**Group—A**  
**(Semiconductor Devices and Circuits)**

Answer any one question.

1. Construct a circuit to study the current-voltage ( $I - V$ ) characteristics curve of a forward biased p-n junction diode. Determine the cut-in-voltage. Calculate the dynamic resistance and compare with theoretical values. (Assume  $\frac{kT}{q} = 0.026 \text{ V.}$ )

(Th-5, Ckt-5, Data-8, Graph-6, Calculation-2+2+2,  
Discussion-5.)

2. Study the reverse characteristics of a Zener diode. Specify the Zener region. Find Zener break-down voltage. Calculate dynamic resistance.

(Th-5, Ckt-5, Data-10, Graph-5, Calculation-2+2+2,  
Discussion-4.)

*(Turn Over)*

3. Study the load regulation curves of a Zener diode considering (a)  $V_S = 1.25 V_Z$  and (b)  $V_S = 1.5 V_Z$  where  $V_S$  = supply voltage,  $V_Z$  = Zener break-down voltage. Calculate the percentage regulation in each case.

(Th-5, Ckt-5, Data-8, Graph-5, Calculation-4+4,  
Discussion-4.)

4. Study line regulation of a Zener diode. Consider two different values of load current. Calculate regulation factor in each case.

(Th-5, Ckt-5, Data-12, Graph-6, Calculation-4,  
Discussion-3.)

5. Construct a full-wave rectifier with a centre-tapped transformer and a  $\Pi$  filter. Plot  $I_L - V_L$  graph for at least two different input voltages. Calculate percentage regulation of the rectifier.

(Th-5, Ckt-5, Data-12, Graph-6, Calculation-4,  
Discussion-3.)

6. Construct the bridge rectifier with a  $\pi$  filter. Plot  $I_L - V_L$  graph for two input voltages. Calculate percentage regulation in both cases.

(Th-5, Ckt-5, Data-12, Graph-6, Calculation-5,  
Discussion-2.)

7. Draw the output characteristic curve of a given n-p-n transistor in CE mode for three different values of base current.

(Th-5, Ckt-5, Data-12, Graph-5, Calculation-4,  
Discussion-4.)

8. Draw the input characteristic curves of the given n-p-n transistor in CE mode for two values of  $V_{CE}$ . Calculate  $h_{ie}$  in each case.

(Th-5, Ckt-5, Data-12, Graph-6, Calculation-4,  
Discussion-3.)

**Group—B****(Instrumentation and Digital Electronics)**

Answer any one question.

9. Construct an astable-multivibrator with 555 timer for a suitable given frequency. Study the waveform on a CRO and measure its duty cycle.

(Th-10, Ckt-10, Data + Calculation of duty cycle-10,  
Discussion-5.)

10. Measure the output offset voltage of an IC-741 OPAMP for different feedback resistance. Implement the circuit on a bread board and show the results.

(Th-8, Ckt-5, Data-14, Calculation-6,  
Discussion-2.)

11. Construct an adder amplifier with IC-741 and measure the output voltage for at least five input voltages. Measure output voltage  $V_s$  in terms of differential input voltages ( $V_+ - V_-$ ).

(Th-10, Ckt-5, Data-10, Graph-5, Calculation-3,  
Discussion-2.)

12. Construct an integrator circuit with IC-741. Measure output voltages for at least five input voltages. Plot output voltage vs. input voltage curve.

(Th-8, Ckt-5, Data-10, Graph-5, Calculation-3,  
Comparison of output voltage with theoretical value-2,  
Discussion-2.)

13. Construct a half-adder circuit with minimum number of gates and verify its operation.

(Th-8, Ckt-6, Ckt implementation-6, Data-10,  
Discussion-5.)

14. For the logic expression :

$$Y = \bar{A}B + \bar{B}A$$

Realise the operation using minimum number of NAND gates only.

Obtain the truth table.

Name the operation performed.

(Th+Ckt-12, Implementation-8, Data-12,  
Discussion-3.)

15. Construct a J-K flip-flop with minimum number of gates and verify its operation.

(Th+Ckt-12, Implementation-10, Data-10,  
Discussion-3.)

16. Design a circuit using available gates to realise the function :

$$Y = (A + BC)(B + \bar{C}A)$$

Obtain its truth table and specify the number of gates required.

(Th+Ckt-12, Implementation-8, Data-12,  
Discussion-3.)

### Marks Distribution

Group A Experiment	:	35
Group B Experiment	:	35
Viva-Voce (10+10)	:	20
Laboratory Note Book (5+5)	:	10

---

Total : 100

---