

Total Pages—7

UG/II/ELECT/H/III/17(Old)

2017

ELECTRONICS

[Honours]

PAPER – III

Full Marks : 100

Time : 4 hours

The figures in the right hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

Illustrate the answers wherever necessary

[OLD SYLLABUS]

GROUP – A


Answer any two questions : 15 × 2

1. (a) State and prove Norton's theorem.

(Turn Over)

(2)

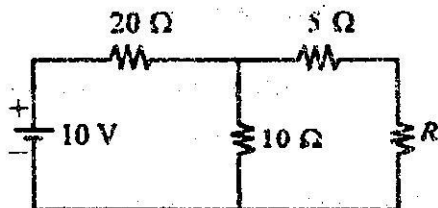- (b) In the following circuit calculate the resistance R which will allow maximum power dissipation in it. Also calculate the maximum power.



- (c) Discuss the principle of operation and applications of Anderson bridge. 5 + 5 + 5
2. (a) Draw the Energy band diagram of a P-N Junction diode. Indicate Fermi level and built-in-potential. Draw again the energy band diagram when a forward voltage V_F is applied.
- (b) Compare Zener break down over Avalanche break down in connection with a P-N Junction.
- (c) Discuss the performance of a P-N junction diode as a half-wave rectifier.

- (d) Explain how a Zener diode can be used as a voltage regulator. $(3 + 2) + 4 + 3 + 3$
3. (a) Explain the principle of operation of a CMOS NAND gate with suitable circuit diagram.
- (b) Discuss with proper circuit diagram how an phase-shift oscillator works.
- (c) Write a short note on IMPATT diode. $5 + 6 + 4$

GROUP – B

Answer any five questions : 8×5

4. (a) Derive the expression for the voltage gain of a feedback amplifier. Hence explain how a feedback amplifier can be converted to an oscillator and derive Barkhausen criteria.
- (b) Write the characteristics of a ideal op-amp. $(3 + 1 + 1) + 3$
5. Explain with a circuit diagram the operating principle of a phase-shaft oscillator. Derive the expression for its oscillating frequency, $5 + 3$

6. Discuss various current components present in a N-P-N Transistor. Prove that

$$I_C = \beta I_B + (1 + \beta) I_{Co} \quad 4 + 4$$

7. For a silicon-controlled rectifier derive the expression of anode current in forward conduction mode. 8
8. Draw the circuit diagram of a common-source *n*-channel JFET amplifier and discuss its small signal operation. Prove that

$$\mu = r_d \cdot g_m \quad 4 + 4$$

9. Discuss how you can derive '*h*' parameters from the input and output characteristics curve of a transistor. 8


10. (a) What are the advantages of *n*-channel MOSFETS over *p*-channel MOSFETS ?

(b) Why ordinary bipolar junction transistors cannot be used at microwave frequencies ?

(c) Explain the rectifying behaviour of a schottky barrier diode with suitable band diagram. 3 + 2 + 3

11. (a) Draw the circuit diagram of an OP-Amp differentiator and derive the expression for its output voltage. Draw the shape of the output signal when a square wave is fed at the input of a differentiator.
- (b) The following circuit is driven by a current source $i = 4\sqrt{2} \sin 314t$ Amp. and is in the steady state. Find the impedance faced by the current source and the power dissipated.

(1 + 1 + 2) + 4

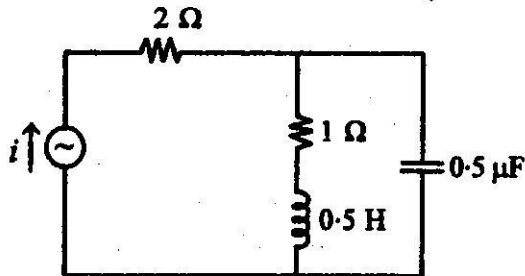


GROUP - C

Answer any five questions :

4 × 5

12. Discuss the working principle of an SMPS. 4

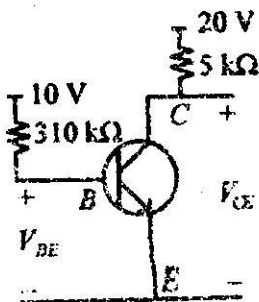13. What do you mean by class A and class B amplifier? What is transformer coupled and what is direct coupled amplifier? 2 + 1 + 1
14. Explain with a neat circuit diagram the principle of operation of an Astable Multivibrator. 4
15. Explain the working principle of a schmitt trigger using an OP-AMP. 4
16. Write a short note on Maxwell's bridge. 4
17. A transistor is operating in the CE mode. Calculate V_{CE} if $\beta = 125$, assume $V_{BE} = 0.6$ V. 4



18. What is a light emitting diode? Why silicon is not preferred as LED material? 4

19. (a) Compare between an emitter follower and a Darlington pair.

(b) What is space charge capacitance? 2 + 2

[*Internal Assessment : 10 Marks*]
