

M.Sc. 1st Semester Examination, 2019

ELECTRONICS

(*Analog circuit and design laboratory*)

(Practical)

PAPER – ELC-106

Full Marks : 50

Time : 3 hours

Answer any **one** question by selecting
through **lucky draw**

1. Design an active low pass filter with the following specifications :

Cutoff freq :- Gain :

Study the performance of the circuit.

2. Design a regulated power supply with the following specifications :
Output voltage : Current :
(to the supplied during examination)

3. Design and study the performance of 2nd order low pass filter with following specifications.
Cut-off frequency :-
Gain :
(to the supplied during examination)

4. Design an active high pass filter. (1st order) with following specification.
Cutoff frequency :-
Gain :
(to the supplied during examination)

5. Design an differential circuit using OP AMP. Take a function and study its performance. Draw the transfer characteristics curve.

(3)

6. Use OPAMP 60 design integrator. Take a function and study its performance in the circuit. Draw the transfer characteristic curve.

7. Design a regulated power supply using OPAMP as comparison.

Outout voltage :

Current :

(to the supplied during examination)

8. Design a fixed biased transistorised circuit and measure V_{CE} , V_{CB} , I_C , I_E at Q point.

9. Design and study the performance of 2nd order high pass filter with folowing specifications.

Cutoff frequency :-

Gain :

10. Design a RC phase shift oscillator and study its performance

frequency :

11. Design a self bias transistorised amplifier and measure V_{BE} , V_{CE} , V_{CB} , I_C , I_B , I_E at Q point. Repeat the same with different BJT.

Distribution of Marks

Experiment	:	35 Marks
Viva-Voce	:	10 Marks
Laboratory Note Book	:	05 Marks
Total		:
		50 Marks