


**2011****MCA****1st Semester Examination****BASIC ELECTRONICS & DIGITAL LOGIC****PAPER—MCA-103***Full Marks : 100**Time : 3 Hours**The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.**Illustrate the answers wherever necessary.***Answer any seven questions.**

1. (a) Distinguish between a metal an insulator and a semiconductor inlight of band theory. 3
- (b) Draw the circuit diagram of bridge rectifier using diodes and briefly explain its operation. 3
- (c) What are the advantages of bridge rectifier over full wave rectifier. 2
- (d) What is ripple factor. 2
2. (a) Establish the relation  $I_c = \beta I_B + (1 + \beta) I_{CBO}$ . 2

*(Turn Over)*

- (b) For a transistor  $\alpha = 0.998$  and voltage drop across  $6k\Omega$  which is connected in the collector circuit is 6 volt. Find the base current for common emitter connection. 3
- (c) Draw the circuit diagram showing the fixed bias of an n-p-n transistor in CE configuration. Derive expressions for its stability factors. 5
3. (a) Draw a neat diagram, properly labelled for obtaining the static characteristics curve of a n channel JFET. 3
- (b) What are the advantages of FET over BJT. 3
- (c) Define "Pinch off voltage" of a JFET. Sketch the depletion region before and after pinch off. (1+1)
- (d) Draw the circuit diagram of MOSFET inverter and explain it. 2
4. (a) Write down the characteristics of an ideal OPAMP. 2
- (b) Derive the expression for the OPAMP used as a differentiator and draw the circuit diagram. 3+2
- (c) What are the advantages of negative feedback over positive feedback. 3
5. (a) Convert the Gray code 101101 into binary code, BCD code and excess 3 code. 3

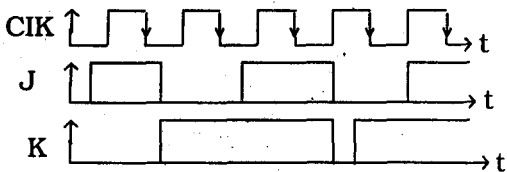- (b) Represent the following numbers in two's complement form +7 and -7. 2
- (c) Design a Gray to Binary code converter. 5
6. (a) Reduce the expression  $\overline{A}BC + B + B\overline{D} + AB\overline{D} + A\overline{C}$ . 3
- (b) What do you mean by cascading of parallel adders? Why is it required? 2
- (c) With the help of a logic diagram explain a parallel adder / subtractor using 2'S complement system. 5
7. (a) Implement the function  $F(D, C, B, A) = \overline{C}BA + D\overline{C}A + D\overline{A}$  using one 8 : 1 Mux and other assorted gates. 6
- (b) Design full subtractor using  $3 \times 8$  decoder. 4
8. (a) What is race-around condition? 2
- (b) The wave forms shown in figure are applied to the negative edge triggered JK flip-flop. Draw the output wave forms.



- (c) Convert D flip flop to JK flip flop. 4

9. (a) Design with proper circuit diagram synchronous 3bit up-down counter using J-K flip-flops. 4+2
- (b) What is the other name of asynchronous counters? Why is that name? 2
- (c) What is the modulus of a counter? 2
10. (a) Design and explain 2 bit magnitude comparator. 4
- (b) What is the difference between EPROM and EAROM. 3
- (c) Write notes on Decimal to BCD encoder. 3

**[ Internal Assessment — 30 ]**

---