

**MCA 1st Semester Examination, 2013**

**BASIC ELECTRONICS AND DIGITAL LOGIC .**

**PAPER —CS/MCA-103**

*Full Marks : 100*

*Time : 3 hours*

**Answer any seven questions**

*The figures in the right-hand margin indicate marks*

*Candidates are required to give their answers in their own words as far as practicable*

*Illustrate the answers wherever necessary*

1. (a) Define the term 'doping'. 2
- (b) Explain the variation of Fermi level with temperature in extrinsic semiconductor. 3
- (c) Explain — "Semiconductors behave as insulator at OK". 2

*( Turn Over )*

- (d) What are the differences between a Zener diode and an ordinary  $p-n$  junction diode. 3
2. (a) Explain briefly the operation of a Bridge rectifier with diagram. What are the advantages of a bridge rectifier as compared to a full wave center tapped rectifier? 5
- (b) Define ripple factor. Calculate its value for half wave and full wave rectifier. 3
- (c) Describe the terms capacitor input filter and inductor input filter. 2
3. (a) Define  $\alpha$  and  $\beta$  of transistor. Find the relation between them. 4
- (b) Explain the input and output characteristics of a transistor in CB configuration. 6
4. (a) Draw the block diagram of a typical op-amp. 3
- (b) Write the characteristics of ideal op-amp. 2
- (c) Derive the expression for the op-amp used as a non-inverting amplifier and draw the circuit diagram. 5

5. (a) Is it possible to produce a junction transistor by connecting two-diode together ? Explain with proper reasoning. 2
- (b) Why biasing is needed ? 2
- (c) A transistor in CE mode configuration the voltage drop across  $5\text{ k}\Omega$  resistance which is connected in the collector circuit is 5 volt. Find the base current. The current gain  $\alpha = 0.998$ . 4
- (d) What are the advantages of negative feedback over positive feedback ? 2
6. (a) Convert the following decimal number to BCD (i)  $2019_{10}$  (ii)  $9701_{10}$ . 2
- (b) What is a Gray Code ? Why it is important ? 2
- (c) Express the function  $Y = A + \bar{B}C$  in canonical POS form. 3
- (d) Using the K-Map method, obtain the minimum sum of product expression of the following function :

$$Y = \Sigma (0, 2, 3, 6, 7, 8, 10, 11, 12, 15) \quad 3$$

7. (a) What is BCD adder. Explain with circuit diagram. 6
- (b) Explain with the help of K-map how we convert BCD to excess 3 code. 4
8. (a) Convert JK flip-flop to D flip-flop. 4
- (b) What is magnitude comparator ? Draw and explain 2-bit magnitude comparator. 5
- (c) Write the applications of comparator. 1
9. (a) Show how the JK flip-flop can be operated as a toggle flip-flop. 3
- (b) Implement the following function using 8 : 1 MUX  $F(A, B, C, D) = [m(0, 7, 8, 9, 10, 11, 15)]$ . 4
- (c) Define race around condition. 3
10. (a) What is decoder ? Implement a full subtractor using 3 : 8 decoder. 4
- (b) Design 3 bit UP-down synchronous counter. 6