

2011

M.Sc.

3rd Semester Examination

ELECTRONICS

PAPER—ELC-306

(PRACTICAL)

Full Marks : 50

Time : 3 Hours

The figures in the right-hand margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

(Electronics and Optical Communication)

Answer any one question.

1. Design a circuit using IC OTA 3080 to generate amplitude modulated signal.

Apply modulating signal of three different amplitude but same frequency. Calculate modulation index for each amplitude of the modulating signal.

Draw a graph to show the variation of modulation index with base band signal amplitude.

(Turn Over)

2. Design a circuit on a bread board using IC 8038 to generate frequency modulation of the signal.
Test the performance of your circuit using a CRO calculate frequency deviation and hence find out the modulation index.
3. Implement a circuit on a bread board using a transistor to generate Pulse Amplitude Modulation (PAM). Observe the PAM output using a CRO. Repeat this for two carrier signal frequency and two modulating signal amplitudes
4. Design and Implement a circuit to generate Pulse Width Modulation using IC555. Record the pulse width of each pulse and the corresponding amplitude of the modulating signal for two different modulating frequencies. For each case plot modulating signal amplitude VS pulse width of the PAM output.
5. Design a circuit for generating DSB-SC signal using diodes. Test the operation of your circuit on a CRO and calculate modulation index for different carrier amplitudes. Take at least three carrier amplitude.
6. Design and implement a DSBSC modulator using IC 1496. Test the operation of your circuit in a CRO and calculate modulation index.

Show the variation of modulation index with base band signal amplitude .

7. Design an envelope detector demodulator circuit for A.M signal. Record the observations of input and output signals for three different modulation. (Implement an AM modulator before demodulation)

Distribution of Marks

Theory	:	05 Marks
Circuit	:	10 Marks
Experiment	:	20 Marks
Result & Discussions	:	05 Marks
Viva-voce	:	05 Marks
Laboratory note book	:	05 Marks
		<hr/>
Total	:	50 Marks
