

**2011****M.Sc.****1st Semester Examination****ELECTRONICS****PAPER—ELC-106****(PRACTICAL)***Full Marks : 50**Time : 3 Hours*

*figures in the right-hand margin indicate full marks.  
Candidates are required to give their answers in their  
own words as far as practicable.*

**(Electronic Circuit Lab)**

*For any one question, selecting it by a lucky draw.*

*Design a regulated power supply using 78xx group  
regulator) and study its performance.*

*Input Voltage = ...V, Output Current = ...mA.*

*Working formula. 4*

*Drawing of circuit diagram with labelling. 3*

*(Turn Over)*

- c) Implementation of the circuit on bread board.
- d) Recording of data for load and line regulation characteristics (one set each). 5+
- e) Drawing of graphs. 4+
- f) Calculation of percentage regulation and stability factor. 2+
- g) Discussion of the results obtained.
2. Design a regulated power supply of variable output using LM317.  
Output Voltage = ...V, Output Current = ...mA.
- a) Working formula.
- b) Circuit diagram with labelling.
- c) Circuit Implementation on bread board.
- d) Recording of data for load and line regulation characteristics (one set each). 5+
- e) Drawing of graphs. 4+
- f) Calculation of percentage regulation and stability factor. 2+
- g) Discussion of the results obtained.

3. Design a regulated power supply using a power transistor as a pass element and an OPAMP as comparator.

Output Voltage = ...V, Output Current = ...mA.

- |   |     |
|---|-----|
| a) Working formula.   | 4   |
| b) Circuit diagram with labelling.  | 3   |
| c) Design <sup>+</sup> considerations and components to be used.                  | 4   |
| d) Circuit Implementation on a bread board.                                       | 4   |
| e) Recording of data for load and line regulation characteristics (one set each). | 4+4 |
| f) Drawing of graphs.   | 3+3 |
| g) Calculation of percentage regulation and stability factor.                     | 2+2 |
| h) Discussion of the results obtained.  | 2   |

4. Design a regulated power supply using power transistor as a pass element and another transistor as a comparator.

Output Voltage = ...V, Output Current = ...mA.

- |   |   |
|---|---|
| a) Working formula.                                 | 4 |
| b) Circuit diagram with labelling.                  | 3 |
| c) Design considerations and components to be used. | 4 |

- d) Circuit Implementation on a bread board.
- e) Recording of data for load and line regulation characteristics (one set each). 4+
- f) Drawing of graphs. 3+
- g) Calculation of percentage regulation and stability factor. 2+
- h) Discussion of the results obtained.
5. Design a low-pass active Butterworth filter with a Roll off rate of 20dB/decade for cut-off frequency = 2 KHz and pass band gain of 1 and study its performance.
- a) Working formula.
- b) Circuit diagram with labelling.
- c) Design considerations for cut-off frequency and pass band gain.
- d) Implementation of the circuit.
- e) Recording of data for frequency response characteristics.
- f) Drawing of graph.
- g) Finding and comparison of Cut-off frequency and Roll-off rate with the supplied value.
- (2+1½)+(2+1½)
- h) Discussion of the results obtained.

6. Design a non-inverting active high-pass filter at a cut-off frequency of 3 KHz and pass band gain of 1 dB using only one R-C section (network) and study its performance.
- |   |                                     |
|---|-------------------------------------|
| a) Working formula.   | 4                                   |
| b) Circuit diagram with labelling.  | 3                                   |
| c) Design considerations for cut-off frequency and gain.  | 4                                   |
| d) Implementation of the circuit.   | 3                                   |
| e) Recording of data for frequency response characteristics.  | 8                                   |
| f) Drawing of graph.  | 4                                   |
| g) Finding and comparison of the Cut-off frequency and Roll-off rate of it with the supplied value. | $(2+1\frac{1}{2})+(2+1\frac{1}{2})$ |
| h) Discussion of the results obtained.  | 2                                   |
7. Design a second order active low-pass Butterworth filter and study its performance.
- |  |   |
|--|---|
| a) Working formula.  | 4 |
| b) Circuit diagram with labelling.   | 3 |
| c) Design considerations for cut-off frequency = _____ Hz and gain = _____ dB. | 5 |

- d) Implementation of the circuit on a bread board
- e) Recording of data for frequency response characteristics.
- f) Drawing of graph.
- g) Finding and comparison of the Cut-off frequency and Roll-off rate of it with the supplied value. (2+1)+1
- h) Discussion of the results obtained.

8. Design a second order active high-pass (Butterworth) using two different R-C sections (Network) and study its performance.

- a) Working formula.
- b) Circuit diagram with labelling.
- c) Design considerations for cut-off frequency = \_\_\_\_\_ KHz and pass band gain = \_\_\_\_\_ dB.
- d) Implementation of the circuit on a bread board
- e) Recording of data for frequency response characteristics and drawing of graph.
- f) Finding and comparison of the Cut-off frequency and the Roll-off rate of it

with the supplied value. (2+1)+(2+1)

g) Discussion of the results obtained. 2

9. Study the performance of a logarithmic amplifier using OPAMP.

a) Working formula. 4

b) Drawing of circuit diagram with labelling. 3

c) Circuit Implementation on bread board. 3

d) Recording of data by varying the input voltage at small steps. 10

e) Drawing of graphs. 4+4

f) Discussion about the nature of curves and the results obtained. 3

g) Comment on possible application of the circuit using the result obtained. 4

10. Study the performance of an antilogarithmic amplifier using OPAMP.

a) Working formula. 4

b) Drawing of circuit diagram with labelling. 3

c) Circuit Implementation on bread board. 3

- d) Recording of data by varying the input voltage at small steps. 10
- e) Drawing of graphs. 4+4
- f) Discussion about the nature of curves and the results obtained. 3
- g) Comment on possible application of the circuit. 4

**Distribution of Marks**

Laboratory note book	:	05 Marks
Viva Voce	:	10 Marks
Experiment	:	35 Marks
<hr/>		
Total	:	50 Marks