

M.Sc. 4th Semester Examination, 2012

ELECTRONICS

(Advanced Electronics Lab)

(Practical)

PAPER—ELC-405

Full Marks : 50

Time : 3 hours

**Answer any one question from either
*PSPICE or Digital Electronics***

The questions are of equal value

*Candidates are required to give their answers in their
own words as far as practicable*

Illustrate the answers wherever necessary

PSPICE

In each of the following questions, you have to save the design file by "your roll no., -design" and then save the plot in a file "your roll no.-plot".

(Turn Over)


Marks Distribution (For PSPICE)

Theory	– 07
Circuit Design	– 10
Simulation	– 10
Verification and Accuracy	– 05
Discussion	– 03
Viva	– 10
Laboratory Note Book	– 05

1. Design an inverting amplifier circuit using op-amp taking input resistor $R_1 = 470 \Omega$, feedback resistor $R_2 = 4.7 \text{ k}\Omega$ and load resistor $R_L = 10 \text{ k}\Omega$. Apply sine wave as an input signal with suitable amplitude and frequency of your choice. Simulate the circuit using PSPICE and plot the input voltage V_{in} versus time and output voltage V_o versus time in the same graph. Also verify the gain of the amplifier with the given value.
2. Design a non-inverter amplifier circuit using op-amp taking input resistor $R_1 = 1 \text{ k}\Omega$, feedback resistor $R_2 = 10 \text{ k}\Omega$ and load resistor $R_L = 10 \text{ k}\Omega$. Apply sine wave as an input signal with suitable amplitude and frequency of your choice. Simulate the circuit using


PSPICE and plot the input voltage V_{in} versus time and output voltage V_o versus time in the same graph. Also verify the gain of the amplifier with given value.

 3. Design an integrator circuit using op-amp taking input resistor $R_1 = 1 \text{ k}\Omega$, feedback resistor $R_2 = 6.8 \text{ k}\Omega$, feedback capacitor $C_2 = 0.1 \text{ }\mu\text{F}$ and load resistor $R_3 = 10 \text{ k}\Omega$. Simulate the circuit using PSPICE and plot the transient response of the output voltage for a duration of 0 to 4 ms in steps of $50 \text{ }\mu\text{s}$ for the input voltage given below.



 4. Design a differentiator circuit using op-amp taking input resistor $R_1 = 1 \text{ k}\Omega$, input capacitor $C_1 = 0.4 \text{ }\mu\text{F}$, feedback resistor $R_2 = 6.8 \text{ k}\Omega$ and load resistor $R_3 = 10 \text{ k}\Omega$. Simulate the circuit using PSPICE and

plot the transient response of the output voltage for duration of 0 to 4 ms in steps of 10 μ s for the input voltage given below.



5. Design a first order low pass active filter with cut-off frequency 3 kHz in PSPICE. Simulate the circuit and plot the gain versus frequency curve. Also verify the cut-off frequency of the plot with its given value.
6. Design a first order high pass active filter with cut-off frequency 1 kHz in PSPICE. Simulate the circuit and plot the gain versus frequency curve. Also verify the cut-off frequency of the plot with its given value.
7. Design a second order active low pass Butterworth filter with cut-off frequency 3 kHz. Simulate the circuit using PSPICE and plot the gain versus frequency curve. Also verify the cut-off frequency with the given value.

8. Design a second order active high pass Butterworth filter with cut-off frequency 1 kHz. Simulate the circuit using PSPICE and plot the gain versus frequency curve. Also verify the cut-off frequency with the given value.
9. Design an astable multivibrator circuit with frequency 1 kHz and duty cycle 66.67% using IC 555. Simulate the circuit using PSPICE and plot the output versus time curve. Also verify the output frequency and duty cycle with the given values.

(Digital Electronics)

Marks Distribution (For Digital)

Theory	— 05
Circuit Design	— 15
Implementation	— 07
Experimental Result	— 05
Discussion	— 03
Viva	— 10
Laboratory Note Book	— 05

10. Design a 4-bit synchronous odd counter using JK flip-flop. Verify the count sequence by LED display.
11. Design a 4-bit synchronous even counter using JK flip-flop. Verify the count sequence by LED display.
12. Design a 4-bit ripple counter using JK flip-flop. Verify the count sequence by LED display.
13. Design a mod 6 synchronous up counter using JK flip-flop. Verify the count sequence by LED display.
14. Design a mod 6 synchronous down counter using JK flip-flop. Verify the count sequence by LED display.