

**M.Sc. 1st Semester Examination, 2012**

**ELECTRONICS**

*( Analog Electronics )*

*( Theory )*

PAPER — ELC- 104

*Full Marks : 50*

*Time : 2 hours*

Answer **Q.No.1** and any **three** from the rest

*The figures in the right hand margin indicate marks  
Candidates are required to give their answers in their  
own words as far as practicable*

*Illustrate the answers wherever necessary*

1. Answer the following : 2 × 5
- (a) With the help of frequency response curve of a first order low pass filter explain its 'roll off rate'.
  - (b) "A class-C amplifier could be used as a power amplifier" — Justify the statement.

*( Turn Over )*

- (c) What do you mean by linear interlaced scanning related to Television ?
- (d) What are voltage and current regulators ?
- (e) Using log and antilog amplifiers how analog division could be obtained ?
2. (a) Deduce expression for output voltage of a differential amplifier using three OPAMPs.
- (b) Draw a suitable circuit diagram and discuss how a second order differential equation could be solved with its help. Indicate the outputs at every stage.
- (c) Draw and label the circuit diagram of an instrumentation amplifier. Explain its operation and advantages. 3 + 3 + 4
3. (a) Draw the circuit diagram of an active low pass second order Butter worth filter and explain its operation. Derive the expression of the transfer function.
- (b) Design an active first order high pass Butter worth filter at cut off frequency 3 kHz and pass band gain 2. (2 + 2 + 3) + 3

4. (a) Give the circuit diagram and describe the operation of a triangular wave generator. Derive the expression for frequency of output signal.
- (b) Describe, with schematic diagram, the operation of a vidicon TV camera. Explain its advantage over the Image Orthicon type Camera.
- 5 + (3 + 2)
5. (a) What do you mean by frequency shift Keying ?
- (b) Discuss how a PLL circuit can be used as a frequency multiplier.
- (c) Indicate how phase detection could be achieved in PLL using XOR phase detector.
- (d) Write down the fundamental differences among class A, class B and class C amplifiers.
- 1 + 4 + 3 + 2
6. (a) What are the advantages of SMPS over an ordinary power supply ?
- (b) Describe how you can generate a variable power supply using ICLM-317. Explain the operation of the circuit used.

(c) Explain with suitable circuit diagram, the principle of operation of a 566VCO.

3 + 3 + 4

*[Internal Assessment – 10 Marks ]*

---