

**M.Sc. 2nd Semester Examination, 2012**

**ELECTRONICS**

*( Digital Electronics )*

**PAPER—ELC-202**

**( Theory )**

*Full Marks : 50*

*Time : 2 hours*

**Answer Q. No. 1 and any three from the rest**

*The figures in the right-hand margin indicate marks*

*Candidates are required to give their answers in their own words as far as practicable*

*Illustrate the answers wherever necessary*

1. (a) Why R-2R ladder type DAC is preferred over a weighted resistor type DAC ? Explain.
- (b) What is burning of EPROM ? How EPROM is erased ?

(c) How many clock are required to convert an analog signal to the digital form using SAR type ADC ?

(d) Give an example of self dual function and prove self duality.

(e) Draw the schematic diagram of a practical sample-and-hold circuit using MOSFET. 2 × 5

2. (a) If  $f = \overline{BC} + (A \oplus B)C$  and  $g = A \oplus B \oplus C$  then using Karnaugh map show that  $f \oplus g = \overline{A} + C$ .

(b) Let  $F = \overline{BCD} + \overline{ABC}\overline{D}$  and  $F_1 = \overline{B} + \overline{CD} + \overline{ACD}$ . Find  $F_2$  such that  $F = F_1 \cdot \overline{F_2}$ . Find the simplest solution of  $F_2$ . 5 + 5

3. (a) What is multiplexer tree ?

(b) Implement the following multi-output combinational logic circuit using 4 to 16-line decoder.

$$F_1 = \sum m(1, 2, 4, 7, 8, 12, 13)$$

$$F_2 = \sum m(2, 3, 9, 11)$$

$$F_3 = \sum m(10, 12, 13, 14)$$

$$F_4 = \sum m(2, 4, 8)$$

(c) Show the schematic diagram, to obtain  $16 \times 8$  memory using  $16 \times 4$  memory ICs. 10

4. Show that the following circuit adds two single binary bits ' $a$ ' and ' $b$ ' with the carry input  $C_{in}$ . Is it possible to avoid using the two inverters at the output of  $z_1$  and  $z_2$  if  $\bar{a}$ ,  $\bar{b}$  and  $\bar{c}_{in}$  are used as inputs. 5 + 5

 


Fig. 1

5. (a) What is charged couple device ? What are the advantages of it over shift register ? State its working principle with suitable diagram.
- (b) Explain with a diagram, the working principle of MOSFET, NOR gate. (1 + 2 + 3) + 4
6. Three partners : Mr. Ajoy, Mr. Bimal and Mr. Chetan decided to select the president of their organization through voting secretly using voting machine among them.
- (a) Develop a appropriate truth table.
- (b) From the results of (a), design a logic circuit that provides an output of logic-1, whenever the majority vote is 'Yes'. Be sure to finish a minimum implementation.
- (c) Modify the logic diagram of voting machine of part (b) so that all 'NOR' gates are used. 4 + 3 + 3

[ Internal Assessment : 10 Marks ]

---