

M.Sc. 1st Semester Examination, 2013

ELECTRONICS

(*Network Analysis and Synthesis*)

[Theory]

PAPER – ELC - 103

Full Marks : 50

Time : 2 hours

Answer **Q. No. 1** and any **three** from the rest


The figures in the right-hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

Illustrate the answers wherever necessary

1. Answer *all* questions : 2 × 5

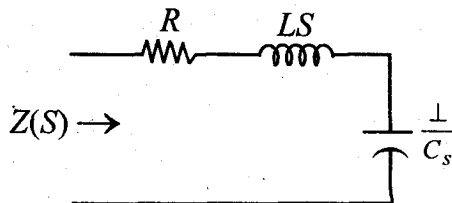
(a) Determine the driving-point impedance of the following Network.




(Turn Over)

(2)

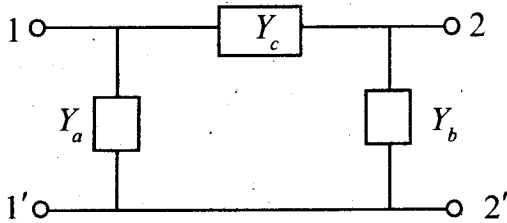
- (b) Find out the admittance matrix of the following circuit.



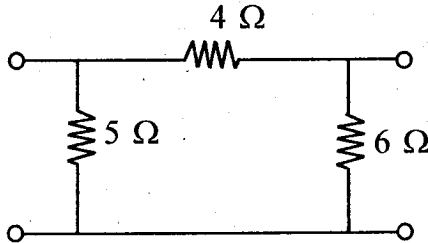- (c) Convert the following π network to an equivalent T network.



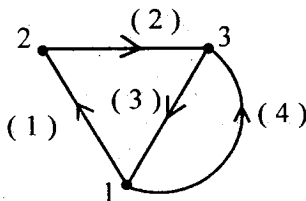
- (d) Determine the number of trees possible for the following graph.




(3)

(e) State and explain the Foster's reactance theorem.

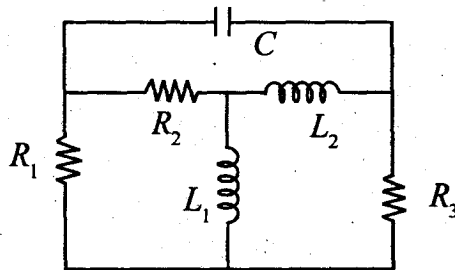2. (a) A network is shown in the following figure. Draw its graph. 2



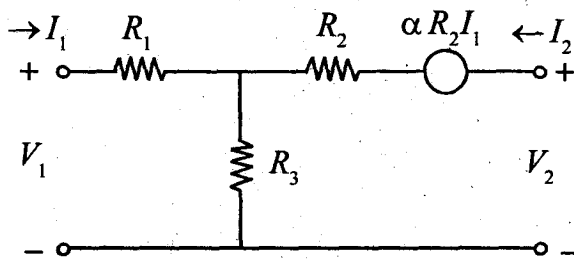
(b) Determine the impedance matrix of the following circuit. 2



- (c) Incidence matrix of a graph is given below.
Draw its directed graph. 4

Nodes	Branches \longrightarrow						
	1	2	3	4	5	6	7
(1)	-1	0	-1	1	0	0	1
(2)	0	-1	0	-1	0	-1	0
(3)	1	1	0	0	-1	1	0
(4)	0	0	1	0	1	0	-1

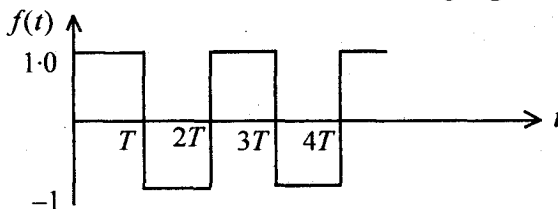
- (d) Find the possible number of trees in a graph for $[A]$ (the reduced incidence matrix) and $[A^t]$ (the transposed matrix of A). 2
3. (a) Define Laplace transformation of a function $f(t)$. 2
- (b) For $f(t) = \cos \omega t$, find $F(s)$. 2
- (c) Obtain the Laplace transform of the square wave train shown in the following figure. 2



(5)

- (d) In the given figure, the battery voltage is applied for a steady state period. Obtain the complete expression for the current after closing the switch K . Assume $R_1 = 1\Omega$, $R_2 = 2\Omega$, $L = 1\text{H}$ and $E = 10\text{ V}$.

4

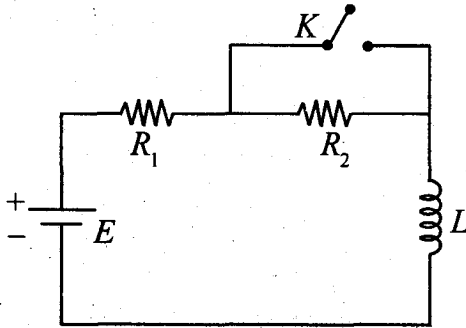

4. (a) Prove that for a reciprocal network

$$AD - BC = 1,$$

where A, B, C, D are different network parameters.


5

- (b) For the network shown below the switch k

(6)

is closed at $t = 0$, determine the current i in the circuit.

5

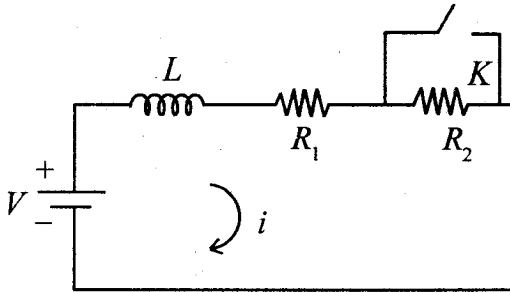

5. (a) Show that the nominal characteristics impedance of a constant K filter is $\sqrt{\frac{1}{c}}$.

5

(b) Design a constant- K low-pass T section filter with a nominal resistance of 50Ω to produce cut off at a frequency 1.2 kHz . Find out the attenuation at 2 kHz frequency.

5

6. (a) Determine the expression for the driving point impedance of a reactive network which has poles at $\omega = 0, 4,000 \text{ rad/s}$ and ∞ , zeros are to be located at $\omega = 2,000$ and $6,000 \text{ rad/s}$. The impedance is to be $-j 700 \text{ ohm}$ at 1000 rad/s .

4

(7)

(b) Find the first Foster network of the driving point impedance function derived earlier. 6

[*Internal Assessment* : 10 Marks]
