

Total Pages—25

PG/IS/ELC-106/13(Pr.)

M.Sc. 1st Semester Examination, 2013

ELECTRONICS

(Electronics Circuit Lab)

(Practical)

PAPER—ELC-106

Full Marks : 50

Time : 3 hours

**Answer any one question, selecting
it by a lucky draw**

The figures in the right-hand margin indicate marks

(Turn Over)

1. Design regulated power supply using 78xx group of IC regulator and study its performance.

Output Voltage = V,

Output Current = mA.

- | | |
|--|-------|
| (a) Working formula. | 4 |
| (b) Drawing of circuit diagram with labelling. | 3 |
| (c) Circuit implementation on breadboard. | 3 |
| (d) Recording of data for getting the characteristic of load and line regulations. | 5 + 5 |
| (e) Drawing of graph. | 4 + 4 |
| (f) Calculation of percentage regulation and stability factor. | 2 + 2 |
| (g) Discuss the results obtained. | 3 |

2. Design regulated power supply using power transistor as pass element and an OP-AMP as comparator.

Output Voltage = ... V, Output Current = ... mA.

- | | |
|--|-------|
| (a) Working formula. | 4 |
| (b) Circuit diagram and labelling. | 3 |
| (c) Design considerations and components to be used. | 4 |
| (d) Circuit implementation on breadboard. | 4 |
| (e) Recording of data for load and line regulations. | 4 + 4 |
| (f) Drawing of graphs. | 3 + 3 |
| (g) Calculation of percentage regulation and stability factor. | 2 + 2 |
| (h) Discussion of the results obtained. | 2 |

3. Study the performance of a logarithmic amplifier using OP-AMP.
- (a) Working formula. 4
 - (b) Circuit diagram with labelling. 3
 - (c) Design considerations and components to be used. 3
 - (d) Recording of data by varying the input voltage at small steps. 10
 - (e) Drawing of graphs. 4 + 4
 - (f) Discuss the nature of the graphic obtained and also the results. 3
 - (g) Comment on possible application of the circuit using the results obtained. 4

4. Design an active low-pass Butterworth filter with a roll off rate 20 dB/decade having cut off frequency 2 kHz and pass band gain of 2. Study its performance.
- (a) Working formula. 4
 - (b) Circuit diagram with labelling. 3
 - (c) Design considerations and components to be used. 4
 - (d) Implementation of the circuit on breadboard. 3
 - (e) Recording of data for frequency response characteristics. 8
 - (f) Drawing of graphs. 4
 - (g) Finding and comparison of cut off frequency and roll-off rate with supplied value.
 $\left(2+1\frac{1}{2}\right)\left(2+1\frac{1}{2}\right)$
 - (h) Discussion of the results obtained. 2

5. Design an active high-pass Butterworth filter with cut off frequency of 3 kHz and pass band gain of 2 using only one R-C section and study its performance.

- (a) Working formula. 4
- (b) Circuit diagram with labelling. 3
- (c) Design considerations and components to be used. 4
- (d) Implementation of the circuit. 3
- (e) Recording of data for frequency response characteristics. 8
- (f) Drawing of graph. 4
- (g) Finding and comparison of the cut-off frequency and roll-off rate with the given values. $\left(2+1\frac{1}{2}\right) + \left(2+1\frac{1}{2}\right)$
- (h) Discussion of the results obtained. 2

6. Design of R-C coupled amplifier using transistors and study its performance.
- (a) Working formula. 4
 - (b) Circuit diagram with labelling. 3
 - (c) Design considerations for gain = 5
 - (d) Implementation of the circuit on bread-board. 3
 - (e) Recording of data for frequency response characteristics. 10
 - (f) Drawing of graph. 4
 - (g) Calculation of bandwidth. 3
 - (h) Discussion of the results obtained. 3

7. Design a second order active high-pass Butterworth filter and study its performance.
- (a) Working formula. 4
 - (b) Circuit diagram with labelling. 3
 - (c) Design consideration for cut off frequency = ... kHz and gain = 2. 5
 - (d) Implementation of the circuit on breadboard. 3
 - (e) Recording of data for frequency response characteristics. 8
 - (f) Drawing of graph. 4
 - (g) Finding and comparison of the cut-off frequency and the roll-off rate with the known values. (2 + 1) + (2 + 1)
 - (h) Discussions of the results obtained. 2

8. Design an active high-pass Butterworth filter at a cut off frequency of 3 kHz and pass band gain of 2 using only one R-C section and study its performance.

- (a) Working formula. 4
- (b) Circuit diagram with labelling. 3
- (c) Design considerations and components to be used. 4
- (d) Implementation of the circuit. 3
- (e) Recording of data for frequency response characteristics. 8
- (f) Drawing of graph. 4
- (g) Finding and comparison of the cut-off frequency and roll-off rate with the given values. $\left(2+1\frac{1}{2}\right) + \left(2+1\frac{1}{2}\right)$
- (h) Discussion of the results obtained. 2

9. Study the performance of an antilogarithmic amplifier using OP-AMP.
- (a) Working principle. 4
 - (b) Drawing of circuit diagram with labelling. 3
 - (c) Circuit implementation on breadboard. 3
 - (d) Recording of data by varying the input voltage at small steps. 10
 - (e) Drawing of graphs. 4 + 4
 - (f) Discussions about the nature of the curves and the results obtained. 3
 - (g) Comment on possible application of the circuit. 4