

**M.Sc. 2nd Semester Examination, 2013**

**ELECTRONICS**

*( Digital Electronics )*

*( Theory )*

PAPER—ELC - 202

*Full Marks ; 50*

*Time : 2 hours*

**Answer Q. No. 1 and any three from the rest**

*The figures in the right-hand margin indicate marks*

*Candidates are required to give their answers in their own words as far as practicable*

*Illustrate the answers wherever necessary*

**1. Answer the following : 2 × 5**

*(a) Draw 'NOT' gate circuit using transistor.*

*(b) How D/A converter is specified ?*

*(c) What is sampling theorem ?*

*( Turn Over )*

- (d) Implement the OR function  $A + B$  using a 2-to-1 MUX.
- (e) What is the difference in the connection between Johnson and Ring counter ?
2. (a) What is the function of Astable multivibrator ?
- (b) What are the advantages of Astable multivibrator over Monostable multivibrator ?
- (c) Draw the schematic diagram of an Astable multivibrator using IC 555 and explain its working principle.
- (d) If the values of the resistances  $R_A = R_B = 1 \text{ k}\Omega$  and the value of the capacitor,  $C$  is  $10 \mu\text{F}$  in Astable multivibrator circuit, find the frequency of the signal generated.  $1 + 2 + 5 + 2$
3. (a) Implement the following multi-output combinational logic circuit using 4 to 16 line decoder.
- $$F_1 = \sum m (2, 4, 8)$$
- $$F_2 = \sum m (1, 3, 5, 7, 9, 11, 13)$$

$$F_3 = \Sigma m (5, 10, 12, 14)$$

$$F_4 = \Sigma m (2, 3, 9, 11, 12, 13).$$

(b) What do you mean by 'Quantization' and 'Encoding'?

(c) To obtain  $16 \times 8$  memory using  $16 \times 4$  memory ICs, find the number of ICs required.

Draw the schematic diagram of the above memory system. 4 + 2 + 4

4. (a) State and prove the Shannon's theorem for getting the canonical SOP form for any  $n$ -variable Boolean function.

(b) Find canonical POS form of the Boolean function  $F = AB + BC + CA$  using Shannon's theorem. 6 + 4

5. (a) Design a combinational circuit using 4 - to - 1 MUX and other necessary logic gates that detects an error by outputting 1 for six non BCD codes and 0 for the BCD codes.

(b) Show that the following circuit designed using MUX can realise any 2-variable function  $f(X_1, X_2)$  where  $f_0 = f(0, 0)$ ,  $f_1 = f(0, 1)$ ,  $f_2 = f(1, 0)$  and  $f_3 = f(1, 1)$ . 5 + 5

6. (a) For a  $n$ -digit number in base  $r$ , the decimal equivalent value is  $N_1$ . If the two digits of positions  $i$  and  $j(j = i - 1)$  are interchanged then the value becomes  $N_2$ . If the sum of the two interchanged digits is  $N_3$ , then show that the digits

$$a_i = \frac{N_3}{2} + \frac{(N_1 - N_2)}{2(r^i - r^{i-1})}$$

$$\text{and } a_j = \frac{N_3}{2} - \frac{(N_1 - N_2)}{2(r^i - r^{i-1})}$$

(b) Explain with suitable diagram the working principle of an R-2R Ladder D/A converter. Find out an expression of output analog voltage as a function of digital inputs.

5 + (2 + 3)

[ Internal Assessment : 10 Marks ]