

Total Pages—7

PG/IIS/ELC-206/13(Pr.)

**M.Sc. 2nd Semester Examination, 2013**

**ELECTRONICS**

*(Electronic Materials and Device Lab)*

( Practical )

PAPER — ELC - 206

*Full Marks : 50*

*Time : 3 hours*

Select any **one** question by lucky draw

1. Implement an adder/subtractor circuit on a bread board using 7483 IC chip. Record your data for two sets of addition of data. During subtraction, subtract one lower number from a higher number and one higher number from the lower number.

( Turn Over )

( 2 )

2. Draw a BCD adder circuit using 7483 IC chip, implement it on the bread board and perform three different BCD addition.

3. Implement the following functions using a 3 : 8 decoder circuits having active low outputs and record the truth table

$$F_1 = \Sigma m (0, 1, 3, 6, 7)$$

$$F_2 = \Sigma m (2, 4, 5)$$

4. Determine the barrier height of a schottky barrier diode, from the thermoionic measurement of the diode current use activation energy measurement method to determine the barrier-height.

5. Apply two different ac signals having frequency 5 kHz and 25 kHz on a diode circuit. Determine the junction capacitance of the device at different applied reverse biases. Plot-C-V characteristics of the device.
  
6. From the current voltage measurement of a P-N junction diode determine the reverse saturation current and material constant of the device.
  
7. Design— a 3 bit R-2R ladder circuit for digital to analog-conversion and verify your result from the recorded data. Plot Analog O/P vs digital input in a mm graph paper.
  
8. Implement the function  $F = \sum m(0, 2, 5, 6, 8, 9)$  on a bread board using 8 : 1 multiplexer and necessary logic gates. Verify your result from the recorded data.

( 4 )

9. Design a 4 bit shift register using J/K F/F on a bread board. Show your result for four sets of data. Draw the corresponding timing diagram.
10. Design a 16 : 1 multiplexer circuit using two 8 : 1 multiplexer and necessary logic gates. Implement this on a bread board and verify the result.

Marks distribution

Theory	:	10
Circuit	:	05
Experiment	:	15
Discussion	:	05
Viva	:	10
LNB	:	05

---

Total : 50 Marks.

---