

M.Sc. 1st Semester Examination, 2015**ELECTRONICS***(Analog Electronics)*

[Theory]


PAPER –ELC - 104

*Full Marks : 50**Time : 2 hours*

Answer Q.No. 1 and any three questions from the rest

*The figures in the right-hand margin indicate marks**Candidates are required to give their answers in their own words as far as practicable**Illustrate the answers wherever necessary*


1. (a) For the circuit shown below.

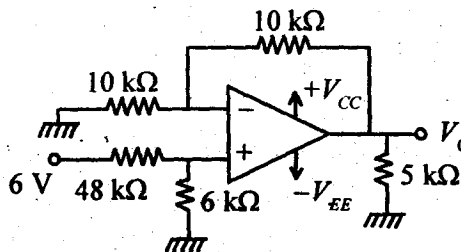Find out the output voltage V_0 .

(Turn Over)

(2)

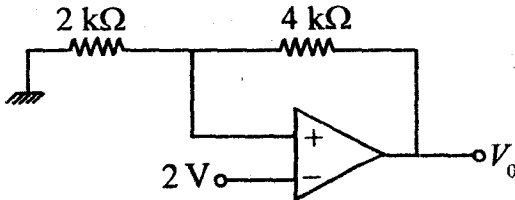- (b) A dc voltage regulator power has a bad regulation $5 \mu\text{r}/\text{mA}$. At no load, output voltage is 10 V. Calculate the output voltage at full load when the full load current is 100 mA.
- (c) "A class-C amplifier could be used as a power amplifier" – Justify the statement.
- (d) A tuned amplifier has maximum voltage gain at a frequency of 2 MHz and the bandwidth is 50 kHz. Find the Q factor.
- (e) Find V_0 of the given circuit-




2 × 5

2. (a) Draw the circuit diagram of a active low-pass second order Butterworth filter and explain its operation. Derive the expression of the transfer function.

(3)

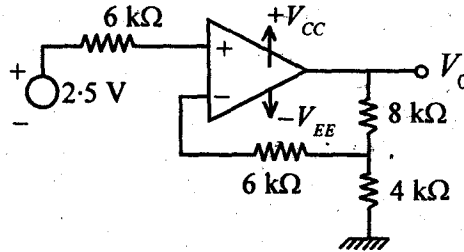- (b) For the circuit shown below find out the value of V_0 .



- (c) Draw the equivalent electrical circuit of a piezoelectric crystal. 5 + 3 + 2
3. (a) Give the block diagram of a standard regulated power supply unit.
- (b) Explain the principle of operation of a series voltage regulator using op-amp.
- (c) Explain a Buck converter using suitable circuit diagram. 2 + 3 + 5
4. (a) Briefly explain the operation of a triangular wave generator with appropriate diagram. Also, derive the expression of o/p signal.

(4)

(b) Explain Schmitt trigger with suitable circuit diagram. Give input and output waveforms.

(4 + 2) + (3 + 1)

5. (a) What do you mean by frequency shift keying?

(b) Discuss how a PLL circuit can be used as a frequency multiplier.

(c) Indicate how phase detection could be achieved in PLL using XOR phase detector.

2 + 4 + 4

6. (a) Draw the circuit diagram of a single tuned amplifier and explain its operation.

(b) Name the basic component of a monochrome television receiver.

(c) In an integrator circuit the time constant is 2 sec. The input is 2 V. dc. Find the output voltage and sketch it.

5 + 2 + 3

[*Internal Assessment* : 10 Marks]
