

**Total Pages—47**

**PG/IS/ELC-106/15 (Pr.)**

**M.Sc. 1st Semester Examination, 2015**

**ELECTRONICS**

*( Electronic Circuit Lab )*

*( Practical )*

**PAPER – ELC-106**

*Full Marks : 50*

*Time : 3 hours*

**Answer any one question, selecting  
it by a lucky draw**

*The figures in the right-hand margin indicate marks*

*( Turn Over )*

SET – I

1. Use LM 317 to design a regulated power supply with following specification

Output Voltage :

Output Current :

[Specification may be provided in the lab during examination]

- |  |       |
|--|-------|
| (a) Working formula.   | 4     |
| (b) Circuit diagram and labelling.                           | 3     |
| (c) Implementation of circuit on breadboard.                 | 3     |
| (d) Record data for load, regulation and line regulation.    | 5 + 5 |
| (e) Draw necessary graphs.                                   | 4 + 4 |
| (f) Calculate percentage if regulation and stability factor. | 2 + 2 |
| (g) Discuss on the results obtained.                         | 3     |

2. Design and study of the performance of a active butter worth low pass filter of the kind of 1st order. Use OPAMP as active element. Specifications :

Cut off frequency . . . . .

Pass band gain . . . . .

[Specifications may be provided in the laboratory during examination.]

Distribution of Marks :

- |   |  |
|---|--|
| (a) Design with working formula.  | 6 + 2                                      |
| (b) Draw the circuit and label.   | 3  |
| (c) Implement the circuit on breadboard.  | 3 + 1                                      |
| (d) Record the data for freq. response.   | 8  |
| (e) Draw the graphs.  | 3  |
| (f) Compare the cut-off frequency and roll-off rate for theoretical and experiment value. | $\left(3\frac{1}{2} + 3\frac{1}{2}\right)$ |
| (g) Discuss on the results obtained.  | 2  |

( 4 )

3. Use 78xx series of IC regulator to design a regulated power supply (fixed) with the following specifications :

Output Voltage : . . . V

Output Current : . . . . mA

[Exact specifications may be provided in the Laboratory]

- |   |       |
|---|-------|
| (a) Design with working formula.                                  | 4     |
| (b) Draw the circuit diagram and label it.                        | 3     |
| (c) Implement the circuit on breadboard.                          | 3     |
| (d) Record the data for load and line regulation characteristics. | 5 + 5 |
| (e) Draw the graphs.  | 4 + 4 |
| (f) Calculate percentage of regulation and stability factor.      | 2 + 2 |
| (g) Discuss on the results obtained.                              | 3     |

( 5 )

4. Use the OPAMP as an antilogarithmic amplifier and study its performance.
- (a) Working principle for design considerations. 4
  - (b) Draw the circuit diagram and label it. 3
  - (c) Implement the circuit on the breadboard. 3
  - (d) Record the output data for variation of input voltage in small steps. 10
  - (e) Draw the graphs. 4 + 4
  - (f) Discuss and comment on the possible application of the circuit. 7

5. Design and study the performance of a regulated power supply. Use power transistor and OP-AMP for design. With following specifications :

Output Voltage : ..... V,

Output Current : ..... mA

- (a) Design consideration with necessary working formula. 8
- (b) Draw circuit diagram and label it. 3
- (c) Implement the circuit on breadboard. 4
- (d) Record data for load and line regulations. 4 + 4
- (e) Draw the necessary graphs. 3 + 3
- (f) Calculate percentage of regulation and stability factor. 2 + 2
- (g) Discuss on the results obtained. 2

6. Design a single stage CE amplifier. Couple the single stage with second stage using Resistance and Capacitance and study its performance.
- (a) Design consideration with working formula. 4 + 4
  - (b) Circuit diagram and labelling. 3
  - (c) Implement the circuit on breadboard. 4
  - (d) Record the data for frequency response characteristics. 10
  - (e) Draw graphs. 4
  - (f) Calculate the Bandwidth. 3
  - (g) Discuss the results obtained. 3

7. Design and study the performance regulated power supply using power transistor as pass element and a transistor as a comparator with following specifications.

Output Voltage : . . . V

Output Current : . . . . mA.

- (a) Working formula with design consideration. 8
- (b) Circuit diagram and labelling. 3
- (c) Circuit implementation on breadboard. 4
- (d) Recording of data for load and line regulations. 4 + 4
- (e) Draw graphs. 3 + 3
- (f) Calculate percentage of regulation and stability factor. 2 + 2
- (g) Discuss the results obtained. 2



8. Design a high pass Butterworth filter using active element with following specifications.

Cut off frequency : .....

Gain : .....

Study its performance.

- |  |       |
|--|-------|
| (a) Working formula with design consideration.   | 9     |
| (b) Circuit diagram and labelling.   | 3     |
| (c) Implement the circuit on breadboard.   | 3     |
| (d) Record of data of frequency response.  | 8     |
| (e) Draw graphs.   | 4     |
| (f) Compare cut-off freq. and roll-off rate between calculated value and experimental value. | 3 + 3 |
| (g) Discuss the results obtained.  | 2     |

( 10 )

9. Use OPAMP as logarithmic amplifier.
- (a) Design consideration and working principle. 4
  - (b) Draw the circuit diagram and label it. 3
  - (c) Implement the circuit on breadboard. 3
  - (d) Record the output data for variation of input voltage in small steps. 10
  - (e) Draw the graphs. 4 + 4
  - (f) Discuss and comment on the possible application of the circuit. 7

10. Design an active low pass first order Butterworth filter with following specifications and study its performance.

Cut off frequency : .....

Gain : .....

- (a) Design consideration with working formula. 9
- (b) Draw the circuit and label. 3
- (c) Implement the circuit on bread board. 3
- (d) Record data for frequency response characteristics. 8
- (e) Draw graphs. 4
- (f) Compare between calculated value and experimental value of cut-off freq. and roll-off rate. 3 + 3
- (g) Discuss the results obtained. 2

11. Design a single stage CE amplifier with following specifications and study its performance.

Gain : . . . . .

- (a) Design consideration and working formula. 8
- (b) Draw circuit diagram and label it and implementation of the circuit on bread-board. 3 + 3
- (c) Record data for frequency chact. 8 + 2
- (d) Draw graphs. 4
- (e) Calculate Bandwidth. 4
- (f) Discuss the results obtained. 3

12. Design an active high pass first order Butterworth filter with following specifications and study its performance

Cut off frequency : . . .

Gain : . . .

- (a) Design consideration with working formula. 8
- (b) Circuit diagram with labelling. 3
- (c) Implementation of the circuit. 3
- (d) Record of data for frequency response characteristics. 8
- (e) Draw graphs. 4
- (f) Compare theoretical value and experimental value of cut-off frequency and roll-off rate.  $\left(3\frac{1}{2} + 3\frac{1}{2}\right)$
- (g) Discuss the results obtained. 2

Distribution of Marks :

Experiment	: 35 Marks
Viva-voce	: 10 Marks
Laboratory Note Book	: 05 Marks
<hr/>	
Total	: 50 Marks

SET – II

1. Design a regulated power supply using a power transistor as a pass element and an OP-AMP as comparator.

Output Voltage : . . . V,

Output Current : . . . mA.

- |  |       |
|--|-------|
| (a) Working formula.   | 4     |
| (b) Circuit diagram with labelling.                            | 3     |
| (c) Design consideration and components to be used.            | 4     |
| (d) Circuit implementation on bread board.                     | 4     |
| (e) Recording of data for load and line regulation.            | 4 + 4 |
| (f) Draw the graphs.   | 3 + 3 |
| (g) Calculation of percentage regulation and stability factor. | 2 + 2 |
| (h) Discuss of the results obtained.                           | 2     |

2. Design a second order active low pass Butterworth filter and study its performance.
- (a) Working formula. 4
  - (b) Circuit diagram with labelling. 3
  - (c) Design consideration for cut-off frequency = . . kHz. 5
  - (d) Implementation of the circuit on bread board. 3
  - (e) Recording of data for frequency response characteristics. 8
  - (f) Drawing of graphs. 4
  - (g) Finding and comparison of the cut-off frequency and roll-off rate with the known values. (2 +1) + (2 +1)
  - (h) Discuss of the results obtained. 2

3. Design a regulated power supply using a power transistor as a pass element and another transistor as a comparator :

Output Voltage : . . . V,

Output Current : . . . mA.

- |   |       |
|---|-------|
| (a) Working formula.  | 4     |
| (b) Circuit diagram with labelling.                                 | 3     |
| (c) Design consideration and components to be used.                 | 3     |
| (d) Circuit implementation on bread board.                          | 3     |
| (e) Recording of data for load and line regulation characteristics. | 4 + 4 |
| (f) Drawing of graphs.  | 4 + 4 |
| (g) Calculation of percentage regulation and stability factor.      | 2 + 2 |
| (h) Discussion of the results obtained.                             | 2     |



4. Design a regulated power supply using 78XX group of IC regulator and study its performance :

Output Voltage : . . . V,

Output Current : . . . mA.

- (a) Working formula. 4
- (b) Drawing of circuit diagram with labelling. 3
- (c) Circuit implementation on bread board. 3
- (d) Recording of data for getting the characteristics of load and line regulation. 5 + 5
- (e) Drawing of graphs. 4 + 4
- (f) Calculation of percentage regulation and stability factor. 2 + 2
- (g) Discussion of the results obtained. 3

5. Design a second order active high pass Butterworth filter and study its performance :
- (a) Working formula. 4
  - (b) Circuit diagram with labelling. 3
  - (c) Design consideration for cut-off frequency .. kHz. 5
  - (d) Implementation of the circuit on bread board. 3
  - (e) Recording of data for frequency response characteristics. 8
  - (f) Drawing of graphs. 4
  - (g) Finding and comparison of the cut-off frequency and roll-off rate with the known values. (2 +1) + (2 + 1)
  - (h) Discuss of the results obtained. 2

6. Study the performance of an antilogarithmic amplifier using OP-AMP.

- (a) Working formula. 4
- (b) Drawing of circuit diagram with labelling. 3
- (c) Circuit implementation on breadboard. 3
- (d) Recording of data by varying the input voltage at small steps. 10
- (e) Drawing the graphs. 4 + 4
- (f) Discussion about the nature of curves and the results obtained. 3
- (g) Comment on possible application of the circuit. 4

7. Design an active high pass Butterworth filter at a cut-off frequency of 3 kHz and pass band gain of 2 using only one R-C section and study its performance :

- (a) Working formula. 4
- (b) Circuit diagram with labelling. 3
- (c) Design consideration and components to be used. 4
- (d) Implementation of the circuit. 3
- (e) Recording of data for frequency response characteristics. 8
- (f) Drawing of graphs. 4
- (g) Finding and comparison of the cut-off frequency and roll-off rate with the given values.  $\left(2+1\frac{1}{2}\right)+\left(2+1\frac{1}{2}\right)$
- (h) Discussions of the results obtained. 2

8. Study the performance of a logarithmic amplifier using OP-AMP.
- (a) Working formula. 4
  - (b) Circuit diagram with labelling. 3
  - (c) Implementation of the circuit on breadboard. 3
  - (d) Recording of data by varying the input voltage at small steps. 10
  - (e) Drawing of graphs. 4 + 4
  - (f) Discuss the nature of graphs obtained and also the results. 3
  - (g) Comment on possible application of the circuit using the results obtained. 4

9. Design a R-C coupled amplifier using transistors and study its performance :
- (a) Working formula. 4
  - (b) Circuit diagram with labelling. 3
  - (c) Design consideration for gain = ... 5
  - (d) Implementation of the circuit on breadboard. 3
  - (e) Recording of data for frequency response characteristics. 10
  - (f) Drawing of graphs. 4
  - (g) Calculation of bandwidth. 3
  - (h) Discussion of the results obtained. 3

10. Design an active low pass Butterworth filter with a roll-off rate 20 dB/decads having cut-off frequency 2 kHz and pass band gain of 2. Study its performance :

- (a) Working formula. 4
- (b) Circuit diagram with labelling. 3
- (c) Design consideration and components to be used. 4
- (d) Implementation of the circuit on breadboard. 3
- (e) Recording of data for frequency response characteristics. 8
- (f) Drawing of graphs. 4
- (g) Finding and comparison of cut-off frequency and roll-off rate with the supplied values.  $\left(2+1\frac{1}{2}\right)+\left(2+1\frac{1}{2}\right)$
- (h) Discussions of the results obtained. 2

11. Design a regulated power supply of variable output using LM 317, output voltage = 5 V to 7.5 V and output current = 100 mA.
- (a) Working formula. 4
  - (b) Circuit diagram with labelling. 3
  - (c) Circuit implementation on breadboard. 3
  - (d) Recording of data for load and line regulation. 5 + 5
  - (e) Drawing of graphs. 4 + 4
  - (f) Calculation of % regulation and stability factor. 2 + 2
  - (g) Discussion on the results obtained. 3

Distribution of Marks :

Laboratory Note Book	: 05 Marks
Viva-voce	: 10 Marks
Experiment	: 35 Marks

Total : 50 Marks