

2019

3rd Semester Examination
ELECTRONICS (Honours)
Paper - C5P
(Semi Conductor Device Lab)

Full Marks : 20

Time : 3 Hours

*The figures in the margin indicate full marks.
Candidates are required to give their answers
in their own words as far as practicable.*

*Answer any one questions selected from lucky draw
questions*

1. Study the forward current voltage characteristics of a P-N junction diode. Draw a graph and calculate the cut-in, voltage, material constant and dynamic resistance from your plot. (Th + Ckt-3, Data Recording-7, drawing of graph-2, Calculations-3)
2. Study the output characteristics of a Bipolar junction Transistor (BJT) operated under common emitter mode for different values of base current. Calculate common

[Turn Over]

emitter current gain from your Plot. (Th + Ckt—3, data recording—8, plotting of graph—2, Calculations—2)

3. Study the current voltage characteristics of a SCR. (Th + Ckt—3, data recording_8, Plotting and Calculations—4)
4. Study the variation of drain current over drain voltage for various gate voltages. Draw a suitable graph and indicate various regions. (Th + Ckt—3, data recording—8, graph and calculation—4)
5. Study the output characteristics of a BJT operated in common base mode and plot your results. Calculate common base current gain and from your plot. (Th+Ckt—3, data recording—8, Plotting of graph and calculation—4)
6. Study the current voltage characteristics of a P-N Junction diode under reverse bias. Plot your data on a graph paper and find out the break down voltage and break down current. (Th + Ckt—3, data recording—8, plotting of graph and calculations—4)
7. Study the current voltage characteristics of a Unijunction Transistor and draw its current voltage curve. Plot your result on a graph paper and indicate

- various regions. (Th + Ckt—3, data recording—8, plotting of graph and calculations—4)
8. Study the I-V characteristics of a MOSFET. (Th + Ckt—3, data recording—8, plotting of graph—4)
 9. Study the input characteristics of a BJT operated in CE mode. Plot your results on a graph paper. (Th + Ckt—3, data recording—8, plotting graph and calculation—4)
 10. Study the Variation of drain current over gate voltage for various drain bias. Plot $\sqrt{I_d} - V_g$ and calculate the threshold voltage of the device from the graph. (Th + Ckt—3, data—8, plotting of graph and calculations—4)

Marks Distribution :

Experiment	: 15 Marks
Laboratory Note Book	: 02 Marks
Viva-vose	: 03 Marks
<hr/>	
Total	: 20 Marks
<hr/>	