

Total Page - 3

UG/3rd Sem/ELEC/(H)/T/19

2019

B.Sc.

3rd Semester Examination

**ELECTRONICS (Honours)**

**Paper - C 6-T**

**(Electronic circuits)**

Full Marks : 40

Time : 2 Hours

*The question are of equal value for any group/half. The figures in the margin indicate full Marks. Candidates are required to give their answers in their own words as far as parctiable. Illustrate the answers wherever necessary.*

1. Answer any five questions : 5×2
  - a) Define Q point in case of a transistor. 2
  - b) Write down two advantages of full bridge rectifier circuit over fullwave centre-tap rectifier. 2
  - c) Define stabilization of a transistor. Mention two techniques of stabilization. 1+1
  - d) Compare performance of different power amplifier in terms of their efficiencies. 2

[ Turn Over ]

(2)

- e) What is the main difference of depletion and enhancement type MOSFET in respect to their construction? 2
- f) Mention two criterion of a circuit being a oscillator. 2
- g) Write down two advantages of CMOS amplifier circuit. 2
- h) What is Miller's effect ?

2. Answer any *four* questions : 4×5 =20

- a) Explain the operation of N-channel enhancement type MOSFET with suitable circuit diagram. 5
- b) Explain the operation of full-wave bridge rectifier circuit using suitable circuit diagram. Give input-output waveform and calculate ripple factor. 2+3
- c) How does BJT work as an amplifier and switch? Explain it using its Voltage transfer curve. 2+3
- d) Define biasing of a transistor. What is stabilization? Why stabilization is required for a transistor. 1+1+3
- e) Differentiate between positive and negative feedback. Mention different types of negative feedback circuit and compare between them. 2+3
- f) Explain working principle of shunt regulated power supply using BJT. 5

(3)

2. Answer any *one* question :

1×10=10

- a) Explain common source amplifier circuit using proper circuit diagram (use small signal equivalent circuit). Deduce input resistance, output resistance and voltage gain. 4+2×3
- b) Explain principle of operation of class-C power amplifier and calculate its efficiency. 5+5
-