

2009**M.Sc.****3rd SEMESTER EXAMINATION****PHYSICS****PAPER—PH-2104****Full Marks : 40****Time : 2 Hours**

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Illustrate the answers wherever necessary.

Module—PH-2104A**(Marks : 20)**

Answer Q. No. 1 and any one from the rest.

1. Answer any five bits : 2×5
- (a) Draw the circuit diagram of a series voltage regulator using OP-AMP as comparator and a transistor as current limiter.
- (b) Draw the circuit diagram of an instrumentation amplifier using 3 OP-AMPs.

(Turn Over)

- (c) Why a logarithmic amplifier cannot be used at very low and very high input voltages ?
- (d) What are the advantages of active filters over passive filters ?
- (e) Explain the advantage of bridge amplifiers over single stage amplifiers.
- (f) Draw the circuit diagram of a square wave generator and write the expression for frequency of oscillation.
- (g) Draw the circuit diagram of an analog multiplier which can multiply both +ve and -ve signals.
2. (a) Explain the operation of a triangular wave generator with proper circuit diagram and derive the expression for the frequency of the output signal. 5
- (b) Explain the operation of a Phase Locked Loop with explanation to its different building blocks. 5
3. (a) Draw and explain the circuit diagram of an antilog amplifier using matched pair of transistors and derive the expression for the output voltage. 5
- (b) Draw the circuit diagram of a 2nd order Low pass Butterworth filter and derive the expression for the transfer function as a function of frequency. 1+4

Module-PH-2104B
(Digital Electronics)

(Marks : 20)

Answer Q. No. 1 and any one from the rest.


1. Answer any five bits : 5×2
- (a) Compare the performance of TTL & CMOS logic gate.
 - (b) Give the basic design of a 24 : 1 MUX using 8 : 1 MUX IC.
 - (c) "CMOS transmission gate" is an ideal switch ; justify.
 - (d) What do you mean by magnetic bubble memory ?
 - (e) Using FPLA memory unit solve the following equations :

$$Y_1 = A B C + \bar{A} B C$$

$$Y_2 = \bar{A} \bar{B} + A C + B C$$

- (f) Give the basic circuit of 2 : 4 decoder.

(g)

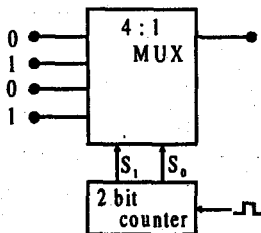

Give the nature of output waveform of the above ckt.

2. (a) Explain the working principle of TTL NAND gate with totempole connection.
- (b) What do you mean by fan-in and fan-out?
- (c) Give the basic difference between encoder and decoder?
- (d) Draw the circuit diagram of a CMOS NAND gate and explain. 4+2+2+2
3. (a) Show the different section of Dynamic RAM unit cell.
- (b) Give example of (i) Optical memory, (ii) Semiconductor memory ; (iii) Magnetic memory & (iv) Sequential memory.
- (c) State briefly the working principle of Magneto-Optical Memory.
- (d) LIFO and FIFO are the examples of shift register. Give comments in support of this statement. 4+2+2+2
-

Module-PH-2104**(Marks : 40)**

Answer Q. No. 1 and any three from the rest.

1. Answer any five bits : 2×5
- (i) Find the band width for a f.c.c crystal along [1 0 0] according to Tight Binding Approximation. 2
- (ii) The energy of formation of vacancy in copper is lev. Estimate the number of vacancy per mole at room temperature. Assume that thermal entropy change is negligible. 2
- (iii) Explain what is meant by Mott's metal & insulator transition. 2
- (iv) What is meant by polarization catastrophe? 2
- (v) The $E - K$ relation in a particular solid is given by $E = Ak^2 + Bk^3$; where A & B are positive constants. Determine the effective mass of the electron at the band bottom.
- (vi) Find the total polarizability of CO_2 , if its susceptibility is 0.985×10^{-3} . Density of carbon dioxide is 1.977 kg/m^3 . 2
- (vii) Why electromagnetic wave cannot excite a plasmon? 2
2. Find the energy spectrum in a solid using nearly free electron approximation & find the energy gap at the zone boundary. 10

3. (a) Derive the LST relation assuming photon-phonon interaction in an ionic crystal. 8
- (b) What is soft optical phonon & what is its significance? 2
4. (a) Derive an expression of ionic conductivity & show that Einstein relation is valid in this case. 5
- (b) Explain with a neat diagram what is meant by Edge dislocation. 3
- (c) Why there is break in $\log D \propto \frac{1}{T}$ curve for an ionic crystal? 2
5. (a) Describe in details Langwin theory & hence find an expression for dipolar polarizability. 5
- (b) Prove that ferroelectric to paraelectric transition in Rochelle salt is second order. 5
6. (a) Describe in details Dehaas Van Alphen effect. What is meant by ultra quantum region? 5+1
- (b) What is Frenkel Exciton? Find the dispersion relation for this case. 4
7. (a) Prove that dielectric loss is related to the imaginary part of the dielectric constant. 3
- (b) Find an expression for Schotky defect in case of an ionic crystal. 3
- (c) Show how polarization direction changes in BaTiO_3 when temperature is lowered. 4