

2009

PHYSICS

PAPER — 1204

Full Marks : 40

Time : 2 hours

The figures in the right-hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

Illustrate the answers wherever necessary

GROUP — A

[*Marks : 20*]

1. Answer any *five* from the following: 2 × 5


- (a) One high-pass filter and one low-pass filter are given. How can you make a band-pass filter by their use jointly?

(Turn Over)

(b) Define reflection coefficient of a transmission line and show that there will be no reflection of the incident wave, if the line is terminated by its characteristic impedance.

(c) A transmission line has the series impedance $Z = \alpha_1 + j\beta_1$ and shunt admittance $Y = \alpha_2 + j\beta_2$. Then obtain the expression of the attenuation co-efficient of the line.

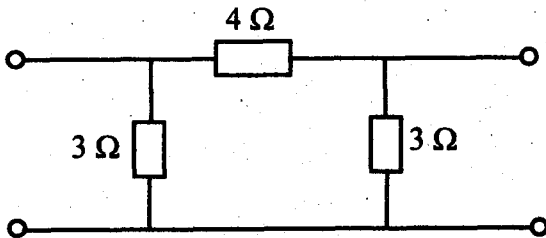
(d) Convert the following π -network into its equivalent T-form.




(e) Define iterative impedance of a T network and find out its expression.

(f) Write the expression of voltage standing wave ratio (VSWR) in case of a transmission line. What information of the line can be obtained from this ratio.

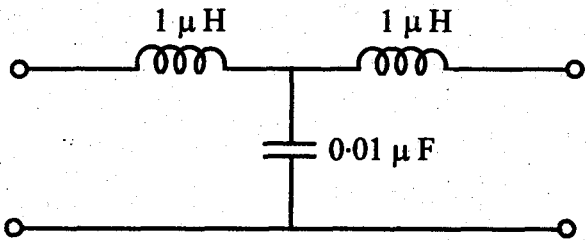(g) Show that the given circuit acts as a constant- k filter. Find out its cut-off frequency.



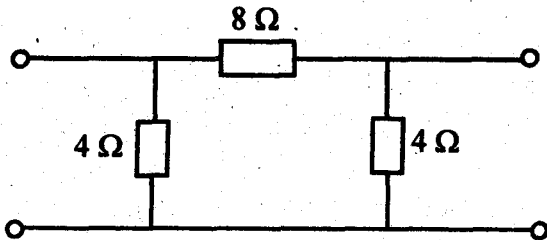(h) Find the characteristic impedance of the circuit.



2. Answer any *one* bit:

10

(a) (i) Discuss the method of reducing a complicated network to a simple T-type network. When can you call a filter active one and when is it passive? 4 + 1

(ii) State and explain the two corollaries of Foster's reactance theorem. 5

(b) (i) Define propagation constant of a transmission line.

(ii) Derive the expression for α and β of a transmission line in terms of the line parameters.

(iii) Explain why frequency and phase distortion occurs in a transmission line.

(iv) Derive the condition of a distortionless line. 1 + 3 + 2 + 4

GROUP—B

(*Digital Electronics*)

[*Marks : 20*]

Answer Q. No. 1 and any *one* from the rest

1. Answer any *five* bits:

2 × 5

(*a*) To signals of 1 kHz and 4 kHz are being applied to the *J* and *K* input of a JK flip-flop respectively. Draw the output waveform with the application of pulse train as a clock pulse.

(*b*) The content of a 4-bit shift-register is initially 1101. The register is shifted six times to the right, with the signal input being 101101, what is the content of the register after each shift.

(*c*) What are the different flags in ALU of 8085 μ P?

(d) What do you mean by the following instructions in 8085 μ P?

(i) STA 2040 H

(ii) SUB B

(iii) ANI OF

(iv) INR A.

(e) Draw the basic structure of a 3-bit PISO register.

(f) For a $32\text{K} \times 20$ memory unit

(i) What should be the length of address bus?

(ii) How many FF are required to store a data taken from this memory?

(iii) What is the capacity of the memory in byte?


(g) What is PROM and what is its difference from ROM?

(h) Why A to D and D to A conversion units are necessary for a microprocessor kit ?

2. (a) You have one serial data 1011. Show clearly how can you get the parallel form of it by the application of clock pulse.

(b) Draw the logic diagram of a 4-bit synchronous up counter and explain its operation with timing diagram.

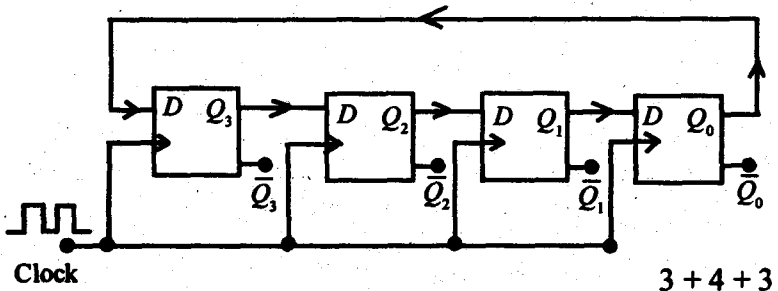(c) Draw the output waveform of Q_3 , Q_2 , Q_1 and Q_0 of the following circuit for 8 consecutive clock pulse.



3. (a) What is the difference between SRAM and DRAM?
- (b) Explain the function of A/D converter with proper circuit diagram.
- (c) Design a monostable multivibrator and explain the working principle.
- (d) Show how to expand a 32×4 RAM unit to 128×8 RAM. 1 + 3 + 3 + 3
-