

M.Sc. 1st Semester Examination, 2012

PHYSICS

(Analog Electronics)

PAPER—PHS-104 (A + B)

Full Marks : 40

Time : 2 hours

Answer Q. No. 1 and any one from each Group

The figures in the right-hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

Illustrate the answers wherever necessary

Use separate scripts for Group—A & Group—B


GROUP – A

[Marks : 20]


1. Answer any five questions : 2 × 5

(a) What is CMRR ? Mention its typical value.

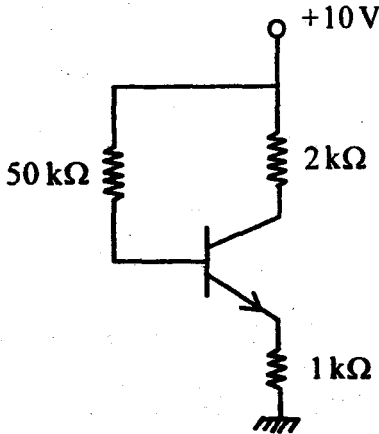- (b) Find the collector current of the silicon transistor of DC current gain 100 from the figure.



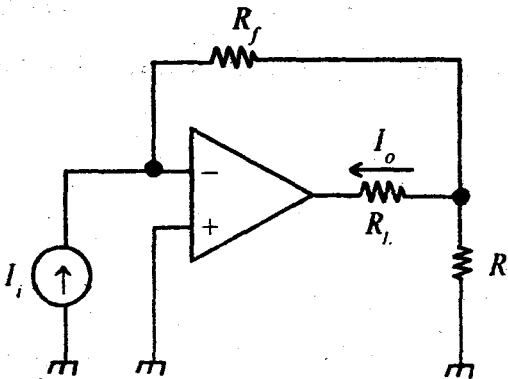- (c) Find out the expression for I_o in terms of I_i and other circuit parameters.



- (d) A 1000 kHz carrier signal is amplitude modulated by audio signals between 100 Hz and 8 kHz. Find
(i) the frequency span of each side band and
(ii) the maximum upper side frequency and the minimum lower side frequency.
- (e) What is a VSB+C type AM signal ? Where is it used ?
- (f) What is Secant law in case of radio wave propagation ?
- (g) Define an array of antenna elements. Why is it used ?
2. (a) Draw the circuit diagram of a current mirror circuit using low β (< 10) *n-p-n* transistors and derive the necessary theory.
- (b) Explain why a constant current source is necessary at the input stage of an op-amp.
- (c) Explain the detailed operation of a super-heterodyne AM radio receiver.
- (d) What are the special characteristics of the diode used for demodulation of AM signal using simple diode detector circuit ? (1 + 3) + 2 + 3 + 1

3. (a) Give a brief account of the effect of the ionosphere on the sky waves. Show that the ionosphere behaves as a medium of refractive index

$$\mu = \sqrt{\frac{1 - 80 \cdot 8 N}{f^2}}$$

where N is electron density per c.c. and f is the frequency in kHz. The effect of the earth's magnetic field and collisions in the ionosphere may be neglected.

- (b) Define skip distance and maximum usable frequency. (2 + 5) + 3

GROUP – B

[Marks : 20]

1. Answer any *five* questions : 2 × 5


- (a) Draw the circuit diagram of a one bit memory cell and write its truth table.
- (b) Minimize the following expression by Karnaugh map :

$$F = ABCD + \bar{A}\bar{B}CD + A\bar{B}\bar{C}D + \bar{A}B\bar{C}D + \bar{A}BCD + A\bar{B}CD + AB\bar{C}D.$$


- (c) Minimize the following expression by Karnaugh map :

$$F = (A + B + C) (\bar{A} + \bar{B} + \bar{C}) (A + \bar{B} + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + C) (\bar{A} + B + C) (A + \bar{B} + C)$$

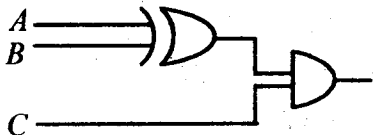- (d) Draw the circuit diagram of a monostable multivibrator with transistors.
- (e) In the logic circuit of a seven segment display there are four input terminals A, B, C & D and seven output terminals Y_1 to Y_7 . Write the necessary truth table to make the circuit active.
- (f) Design the following circuit with NAND gate only.




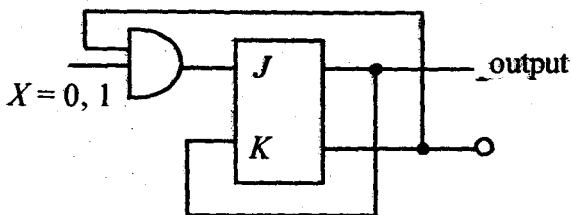- (g) What will be the output with the application two consecutive clock pulses ?



2. (a) What is a shift register ? Discuss the process developing a serial-in serial-out shift register by supporting flip-flops.
- (b) What do you mean by a serial-in parallel-out shift register ? Discuss it with proper circuit diagram
- (c) Write the advantage of serial-in parallel-out shift register over serial-in serial out one. 4 +
3. (a) Solve the following digital equation using K' map
- $$Y = LTP + \bar{L}TW + \bar{L}\bar{T}P + \bar{L}\bar{W}T$$
- (b) What is the difference between astable and monostable multivibrator ? Give example.

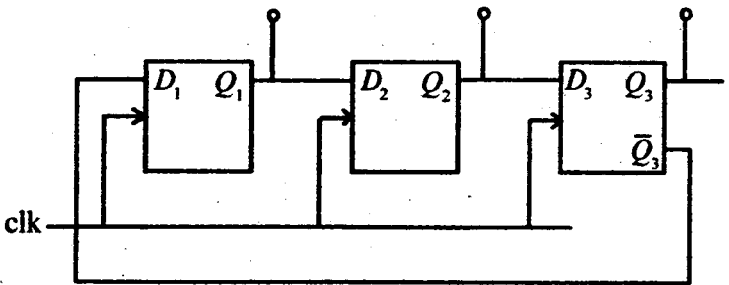- (c) Design 3 bit up/down asynchronous counter with a mode selector which can control the 'up' or 'down' direction.
- (d) Give the different state of the following circuit.



$3 + 2 + 3 + 2$