

2022

1st Semester Examination

ELECTRONICS

Paper : ELC 103

(Network Analysis and Synthesis)

Full Marks : 40

Time : Two Hours

*The figures in the margin indicate full marks.
Candidates are required to give their answers
in their own words as far as practicable.*

Answer any *four* questions each from Group-A and Group-B; and *two* questions from Group-C.


Group - A

Answer any *four* questions : $2 \times 4 = 8$

1. State the superposition theorem. 2
2. Define the terms loop, tree, link and twig. $\frac{1}{2} \times 4$
3. A, π network has the arm impedances $2k\Omega$, $3k\Omega$ and $5k\Omega$ respectively. Calculate the arm impedance of the respective T network. 2

P.T.O.

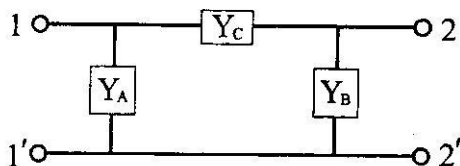4. Find out the y matrix of the following network. 2




5. Let us consider the identify $P(S) = (S + 1) (S + 2) (S + 3) (S + 4)$, where $P(s)$ is the denominator polynomial of a network function, comment on the stability of the network considering R-H criteria. 2
6. Find out the Laplace transform of $u(t - a)$. 2

Group - B

Answer any *four* questions : 4×4=16

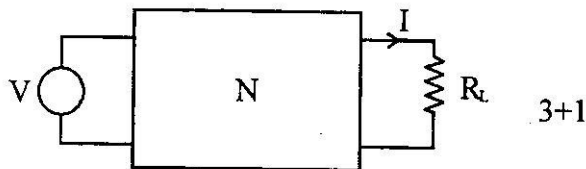7. The network N , contains linear, passive and bilateral elements. When $R_L = 1.5 \Omega$, $I = 2A$ and when $R_L = 4 \Omega$, $I = 1A$, Determine R_L , so that maximum power is dissipated in it. What is the maximum power?



8. The reduced incidence matrix of an oriented graph is

$$[A] = \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$


Draw the network graph.

(3)


9. Prove that for a reciprocal network $AD - BC = 1$, where A, B, C and D are the transmission parameters of the network. 4
10. Find the first Foster network of the driving point impedance function 4

$$z = j0.1 \omega \frac{(\omega^2 - 4 \times 10^6)(\omega^2 - 36 \times 10^6)}{\omega^2(\omega^2 - 16 \times 10^6)}$$

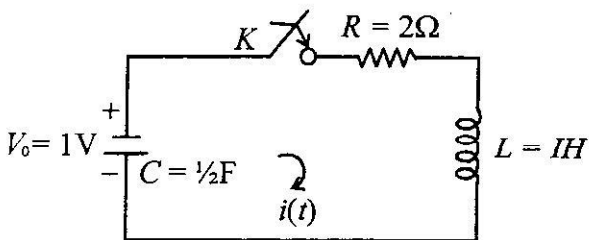11. For the following R-L-C circuit, the capacitor initially charged to a voltage v_0 . Find expression for the current through resistance R , $i(t)$. 4



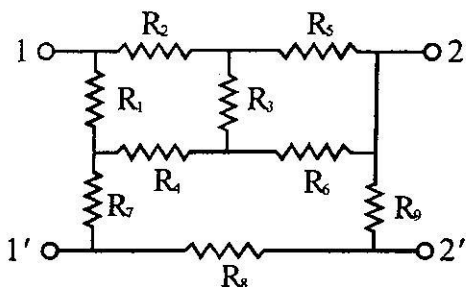12. Reduce the following circuit to an equivalent T network. 4




P.T.O.

Group - C


Answer any *two* questions.

8×2=16

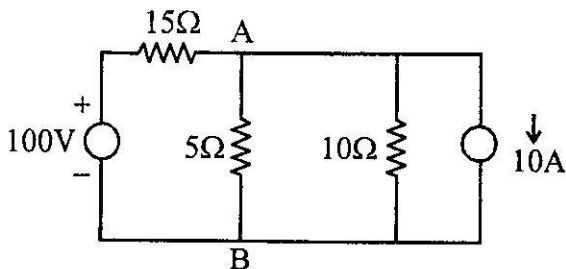13. (a) Using Thevenin's theorem determine the current in the branch AB of the following circuit.



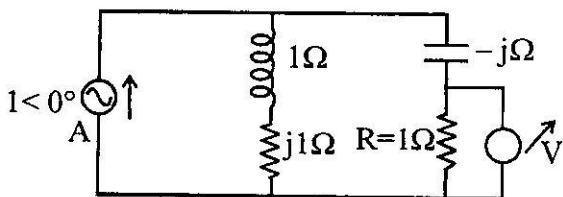- (b) In the given circuit, find the reading of the voltmeter V . Interchange, the current source and the voltmeter and verify the reciprocity theorem.




4+4

14. (a) Prove that
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$

$[A_a, B_a, C_a, D_a]$, $[A_b, B_b, C_b, D_b]$, $[A, B, C, D]$ are the transmission parameters of network N_a , N_b and N respectively and the networks N_a and N_b are in cascade to form network N .

- (b) Prove that if N_a and N_b are connected in parallel, the y parameters of the combined network N will be the sum of the respective y parameters of network N_a and N_b . 4+4

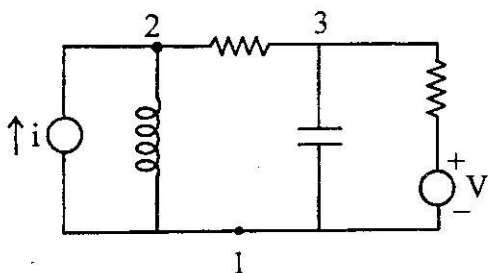15. (a) How many trees are possible for the graph of the network given below :



- (b) For a linear, bilateral passive two port network prove that $\Delta z \Delta y = 1$ where Δy and Δz represent the determinant of y and z matrix of the network respectively. 3+5
16. (a) State the Foster reactance theorem.
- (b) A reactance function has zero at $\omega_1 = 10^5$ rad/s and infinity. It has poles at $\omega = 0$, and $\omega_2 = 1.1 \times 10^5$ rad/s. The slope of the reactance curve is required to be $0.1 \Omega \text{ rad}^{-1} \text{ s}$ at $\omega = 10^5$ rad/s. Find a reactance network satisfying this requirement. 2+6