

M. Sc. 3rd Semester Examination, 2023**ELECTRONICS***(Introduction to Electronics)*

PAPER — ELC-304 (CBCS)

*Full Marks : 50**Time : 2 hours**The figures in the right hand margin indicate marks**Candidates are required to give their answers in their own words as far as practicable***GROUP—A**Answer any **four** questions : 4 × 2

1. Find the value of $(1100)_2 - (0011)_2$. 2
2. What are simplex & full duplex communication system? 1 + 1

3. What are set up time & holding time in connection with cellular communication system? $1 + 1$
4. Write the truth table of NOR & NAND gates. Why are they called universal gates? $(\frac{1}{2} + \frac{1}{2}) + 1$
5. What are pure & impure semiconductors? $1 + 1$
6. Find the value of $(356)_8 + (123)_8$. 2

GROUP - B

Answer any **four** questions : 4×4

7. Why do modulation is required & what are the advantages of modulation ? Draw the envelopes of FM & AM modulated wave. $1+1+1+1$
8. Draw the output characteristics of BJT in CE mode. Show its different regions. $2 + 2$

9. Draw the circuit diagram of a full wave rectifier & explain its operation. 1 + 3
10. Design a full adder circuit. 4
11. What is Morr's law with reference to IC design.
What are SSI, MSI, LSI, VLSI & SLSI ?
12. Write down De Morgan's theorem. $2 + (\frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2})$
4

GROUP - C

Answer any **two** questions : 2 × 8

13. Design a MOD-8 Counter. 8
14. Draw the circuit diagram of a J-K flip flop & write down the truth table. What is race around condition & how it can be overcome ? 2+2+2+2
15. What is hands off process in cellular communication system? Describe the hands off process briefly. 2 + 6

16. What is doping? Draw the forward bias and reverse bias characteristics of a p-n Junction diode. What is knee voltage? 2 + 2 + 2 + 2

[Internal Assessment – 10 Marks]
