

M.Sc. 2nd Semester Examination, 2023

ELECTRONICS

PAPER – ELC-203


Full Marks : 50

Time : 2 hours

The figures in the right hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

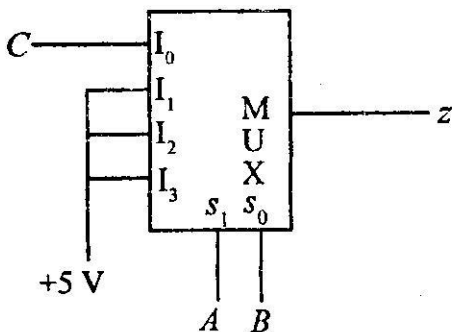1. Answer any *four* questions : 2 × 4
- (a) Implement NAND gate using diode and transistor only.
 - (b) Implement XOR gate using NOR only.
 - (c) The MUX shown below is a 4×1 multiplexer. Find out the output of the following :



(d) Differentiate between synchronous and asynchronous counter.

(e) Prove that $A + BC = (A + B)(A + C)$.

(f) What is the advantage of ECL circuit ?

2. Answer any *four* questions : 4 × 4

(a) Simplify the Boolean expression using k-map.

$$F = \bar{A} + AB + ABD\bar{D} + A\bar{B}\bar{D} + C \quad 4$$

(b) Implement full adder circuit using 4×1 MUX. 4

(c) Design 4-bit magnitude comparator circuit. 4

(d) Convert SR F/F to JK F/F. 4

(e) Design Ring counter and mention its different state. 2 + 2

(f) Write Totem-pole configuration of TTL NAND gate. 4

3. Answer any *two* questions : 8 × 2

(a) Design MOD-10 synchronous counter. 8

(b) Write short notes on SAR A/D converter circuit. 8

(c) Design a counter which counts (0, 2, 4, 5, 7, 8, 9 and 0). 8

(d) Write short notes on different types of shift registers. 8

[Internal Assessment – 10 Marks]
